

National Sun Yat-sen University
Department of Electrical Engineering

114-2 Practical Digital System Design

HW2 Voting and Median Circuit Design

Name: Enping, Chung

Student ID: B133015012

Table of Contents

Part I.Voting

I.Design Process

II.Design Comparison

III.Testbench

IV.Waveform Analysis

V.Circuit Analysis

PART II. Median

I.Design Process

II.Testbench

III.Waveform Analysis

IV.Circuit Analysis

III.Experience and Reflection

Part I. Voting

I. Design Process

Goal : A voting circuit of this type takes five 5-bit one-hot inputs, where each input has exactly one bit set to logic 1, representing a selected position. The circuit first uses combinational logic, such as adders, to count how many times each bit position is selected across the five inputs, effectively generating five vote totals. These totals are then compared using comparators to determine which position has the highest count. In cases where two or more positions have equal counts, an arbitration or priority mechanism is applied to select one based on a predefined rule, typically favoring the higher-order bit. Once the winning position is identified, encoding and decoding logic (or multiplexers) are used to produce a 5-bit one-hot output corresponding to that position, while the associated vote total is converted into a 3-bit binary value representing how many times that input occurred.

Design I

Design I works by first counting how many times each bit position is selected across the five one-hot inputs, then choosing the position with the highest count and outputting both that position and its frequency. Specifically, it begins by computing five separate vote counts, one for each bit position (from bit 0 to bit 4), where each count represents how many inputs have a logic 1 in that position. This counting process can be viewed as a set of parallel addition functions, where each function sums the corresponding bits from all inputs, such as:

$$c0 = a0[0] + a1[0] + a2[0] + a3[0] + a4[0]$$

$$c1 = a0[1] + a1[1] + a2[1] + a3[1] + a4[1]$$

$$c2 = a0[2] + a1[2] + a2[2] + a3[2] + a4[2]$$

$$c3 = a0[3] + a1[3] + a2[3] + a3[3] + a4[3]$$

$$c4 = a0[4] + a1[4] + a2[4] + a3[4] + a4[4]$$

After obtaining these counts, the algorithm performs a comparison function to determine the maximum value among them. This can be interpreted as a max-selection function:

$$\text{max_count} = \max(c0, c1, c2, c3, c4)$$

If multiple positions have the same highest count, a priority selection function is applied that favors the higher-indexed bit. This priority logic ensures deterministic behavior and can be expressed as a sequence of conditional comparisons starting from the highest bit:

if ($c4 \geq c3, c2, c1, c0$) select bit 4


else if ($c3 \geq c2, c1, c0$) select bit 3

else if ($c2 \geq c1, c0$) select bit 2

else if (c1 >= c0) select bit 1

else select bit 0

Finally, an encoding function converts the selected bit position into a one-hot 5-bit output, while a routing function assigns the corresponding vote count to the output

 

Design II

Design II implements a combinational 5-input voting circuit that takes five 5-bit one-hot inputs and determines which bit position (0–4) is selected most frequently. Each input is first converted from a one-hot vector into a 3-bit index representing the active bit position. The design then computes five vote counts, where each count represents how many of the inputs correspond to a given index from 0 to 4. After obtaining these counts, a tournament-style comparison tree is used to find the maximum value efficiently by comparing pairs of counts step by step until a final winner is selected. If two counts are equal, a tie-breaking rule is applied that selects the higher index to ensure deterministic behavior. The `max2_pick` module performs each pairwise comparison by choosing the larger count and, in the case of a tie, the larger index. Finally, the winning index is converted back into a one-hot 5-bit output using a left shift operation, and the corresponding maximum count is assigned to the count output, producing both the most popular bit position and its frequency.

II.Design Comparison

Design II is better than Design I because it replaces the brute-force bit-column adders plus a long priority if/else chain with a more structured datapath: it first encodes each one-hot input into a 3-bit index, then computes bucket tallies using parallel equality checks, and finally selects the winner with a small 4-stage max tournament (`max2_pick`). This makes the design more regular, easier to synthesize for speed, and avoids the wide multi-way comparisons of the original code, while preserving the same tie rule and I/O behavior.

III. Testbench

The testbench first defines the inputs, outputs, and extra signals used for verification. The outputs from the UUT are out (the winning one-hot bit position) and count (how many inputs voted for that position). It also defines expected values (exp_out, exp_count) and counters to track total tests and errors. The main verification logic is in calculate_expected_value, which simulates the voting process in software. It counts how many inputs select each bit position (0 to 4), then chooses the highest count. If there is a tie, the higher bit position wins because of the priority order in the if-else chain. It then sets the expected output and count. The run_all_cases run first, using a For loop, all legal inputs are tested with no delay. Then, run_case task applies inputs to the UUT, computes the expected result, waits for the circuit to settle, and compares the UUT output with the expected values. It prints PASS if they match or FAIL if they don't, while also tracking errors. Finally, the initial block runs multiple test cases, including normal, edge, and corner cases, and prints a summary of results at the end. Overall, the testbench verifies that the voting circuit behaves correctly under all conditions, including tie-breaking scenarios.

Terminal output:

[ALL CASES]-----											
ALL SUMMARY: PASS (3125 tests)											
[SELECTED CASES]-----											
time	a0	a1	a2	a3	a4	exp_out	out	exp_count	got_count	Result	Description
[MAIN FUNCTION CASES]-----											
10	10000	10000	10000	01000	00001	10000	10000	3(011)	3(011)	PASS	main_1_example_from_TA
20	00010	00010	00010	00010	00100	00010	00010	4(100)	4(100)	PASS	main_2_clear_majority
30	10000	01000	00100	00001	00001	00001	00001	2(010)	2(010)	PASS	main_3_three_way_bottom
[EDGE CASES]-----											
40	10000	01000	00100	00010	00001	10000	10000	1(001)	1(001)	PASS	edge_1_all_candidates_tie
50	10000	10000	01000	01000	00001	10000	10000	2(010)	2(010)	PASS	edge_2_two_way_top_tie
60	00001	00001	00001	00001	00001	00001	00001	5(101)	5(101)	PASS	edge_3_all_same
[CORNER CASES]-----											
70	00001	00001	00001	00001	00001	00001	00001	5(101)	5(101)	PASS	corner_1_lowest_unanimous
80	00010	00010	00001	00001	00100	00010	00010	2(010)	2(010)	PASS	corner_2_low_bit_tie
90	10000	01000	00100	00100	00010	00100	00100	2(010)	2(010)	PASS	corner_3_valid_spread_repea
SUMMARY: PASS (9/9)											

IV. Waveform Analysis

(10=10000, 08=01000, 04=00100, 02=00010, 01=00001)

Main Function Cases:

a0[4:0] =10	10		
a1[4:0] =10	10		
a2[4:0] =10	10		
a3[4:0] =08	08		
a4[4:0] =01	01		
out[4:0] =10	10		
count[2:0] =01	011		

a0 = 10000 a1 = 10000 a2 = 10000

a3 = 01000 a4 = 00001

out = 10000 count = 3

main_1_example_from_TA

a0[4:0] =02	02		
a1[4:0] =02	02		
a2[4:0] =02	02		
a3[4:0] =02	02		
a4[4:0] =04	04		
out[4:0] =02	02		
count[2:0] =10	100		

a0 = 00010 a1 = 00010 a2 = 00010

a3 = 00010 a4 = 00100

out = 00010 count = 4

main_2_clear_majority

a0[4:0] =10	10		
a1[4:0] =08	08		
a2[4:0] =04	04		
a3[4:0] =01	01		
a4[4:0] =01	01		
out[4:0] =01	01		

a0 = 10000 a1 = 01000 a2 = 00100

a3 = 00001 a4 = 00001

out = 00001 count = 2

main_3_three_way_bottom

Edge Cases:

a0[4:0] =10	10		
a1[4:0] =08	08		
a2[4:0] =04	04		
a3[4:0] =02	02		
a4[4:0] =01	01		
out[4:0] =10	10		
count[2:0] =00	001		

a0 = 10000 a1 = 01000 a2 = 00100

a3 = 00010 a4 = 00001

out = 10000 count = 1

edge_1_all_candidates_tie

a0[4:0] =10	10		
a1[4:0] =10	10		
a2[4:0] =08	08		
a3[4:0] =08	08		
a4[4:0] =01	01		
out[4:0] =10	10		
count[2:0] =01	010		

a0 = 10000 a1 = 10000 a2 = 01000

a3 = 01000 a4 = 00001

out = 10000 count = 2

edge_2_two_way_top_tie

a0[4:0] =01	01		
a1[4:0] =01	01		
a2[4:0] =01	01		
a3[4:0] =01	01		
a4[4:0] =01	01		
out[4:0] =01	01		
count[2:0] =10	101		

a0 = 00001 a1 = 00001 a2 = 00001

a3 = 00001 a4 = 00001

out = 00001 count = 5

edge_3_all_same

Corner Cases:

a0[4:0] =01	01		
a1[4:0] =01	01		
a2[4:0] =01	01		
a3[4:0] =01	01		
a4[4:0] =01	01		
out[4:0] =01	01		
count[2:0] =10	101		

a0 = 00001 a1 = 00001 a2 = 00001

a3 = 00001 a4 = 00001

out = 00001 count = 5

corner_1_lowest_unanimous

a0[4:0] =02	02		
a1[4:0] =02	02		
a2[4:0] =01	01		
a3[4:0] =01	01		
a4[4:0] =04	04		
out[4:0] =02	02		
count[2:0] =01	010		

a0 = 00010 a1 = 00010 a2 = 00001

a3 = 00001 a4 = 00100

out = 00010 count = 2

corner_2_low_bit_tie

a0[4:0] =10	10		
a1[4:0] =08	08		
a2[4:0] =04	04		
a3[4:0] =04	04		
a4[4:0] =02	02		
out[4:0] =04	04		
count[2:0] =01	010		

a0 = 10000 a1 = 01000 a2 = 00100

a3 = 00100 a4 = 00010

out = 00100 count = 2

corner_3_valid_spread_repeat

V.Circuit Analysis


For circuit analysis, since both designs were written in behavior level, we used open source program Yosys to synthesize the circuit and estimate the amount of logic gates used.

For Design I

Terminal Output:

```
=== voting ===
+-----Local Count, excluding submodules.
|
607 wires
633 wire bits
230 public wires
256 public wire bits
7 ports
33 port bits
377 cells
113 $and
12 $mux
154 $not
38 $or
60 $xor
```

Longest Critical Path:

 

For Design II

Terminal Output:

```
=== design hierarchy ===
+-----Count including submodules.
|
316 voting
40 max2_pick
+-----Count including submodules.
|
316 wires
416 wire bits
44 public wires
144 public wire bits
31 ports
105 port bits
- memories
- memory bits
- processes
316 cells
80 $_ANDNOT_
48 $_MUX_
22 $_NAND_
15 $_NOR_
2 $_NOT_
42 $_ORNOT_
38 $_OR_
21 $_XNOR_
48 $_XOR_
4 submodules
4 max2_pick
```

PART II. Median

I.Design Process

Goal : The median module takes five 6-bit inputs and analyzes them bit-by-bit across all five values. For each bit position (0 to 5), it first counts how many of the five inputs have a logic '1' at that position (s0 to s5). It then forms a cumulative sum across bit positions (c0 to c5), effectively building a running total of how many ones have been seen up to each bit index. Finally, it generates a one-hot 6-bit output where exactly one bit is set: the output indicates the first bit position where the cumulative count reaches or exceeds 3 (a majority of the five inputs). In other words, the module finds the “median” bit position in terms of where the majority of ones are concentrated across the inputs.


Design

The module is designed to take five 6-bit inputs and produce a 6-bit one-hot output that indicates the “median position” based on where the accumulation of 1s crosses a midpoint threshold.

First, the design treats each bit position independently. For each of the six bit positions (from bit 0 to bit 5), it counts how many of the five inputs have a logic 1 in that position. This produces six small count values, each representing how many inputs are “active” in that bit position.

Next, instead of stopping at these individual counts, the design builds a running cumulative total across bit positions. Starting from bit 0, it progressively adds the counts from lower to higher bit positions. This creates a prefix-style accumulation that represents how many total 1s have appeared up to each bit position.

 Finally, the output is generated by finding the first bit position where this cumulative total reaches or exceeds the value 3. Since there are five inputs, 3 represents the majority (or median threshold). The output is one-hot, meaning only one bit is set to 1, corresponding to the first position where the accumulated count crosses this threshold.



II. Testbench

The testbench first defines the inputs, outputs, and signals used for verification. The inputs are five 6-bit one-hot values (a0 to a4), and the output out is the median result in one-hot form. It also defines expected values (exp_out, exp_med) and counters for total tests and errors.

The main verification logic is in calculate_expected_value, which acts as a golden model. It counts how many inputs select each value (0–5), forming a histogram, then computes cumulative sums. The median is chosen as the smallest value where the cumulative count reaches at least three, since there are five inputs. This value is then converted back to one-hot form for comparison.

The run_all_cases task performs exhaustive testing using nested loops to try all possible input combinations, ensuring full coverage of the design.

The run_case task applies specific inputs, computes the expected result, waits for the circuit to settle, and compares it with the DUT output. It prints PASS or FAIL and updates the error count.

Finally, the initial block runs directed, edge, and corner cases, then prints a summary of results. Overall, the testbench verifies correct median behavior for all input conditions.

Terminal output:

[ALL FUNCTION CASES]-----											
ALL SUMMARY: PASS (7776 tests)											
[SELECTED CASES]-----											
time	a0	a1	a2	a3	a4	exp_out	out	exp_med	got_med	Result	Description

[MAIN FUNCTION CASES]-----											
10	100000	100000	010000	000100	000001	010000	010000	4(100)	4(100)	PASS	main_1_example_from_TA
20	000001	000010	000100	001000	010000	000100	000100	2(010)	2(010)	PASS	main_2_sorted_unique
30	000100	000100	000100	100000	000001	000100	000100	2(010)	2(010)	PASS	main_3_clear_middle_repeat
[EDGE CASES]-----											
40	000001	000001	000001	000001	000001	000001	000001	0(000)	0(000)	PASS	edge_1_all_same_lowest
50	100000	100000	100000	100000	100000	100000	100000	5(101)	5(101)	PASS	edge_2_all_same_highest
60	000001	000010	000100	001000	100000	000100	000100	2(010)	2(010)	PASS	edge_3_wide_spread
[CORNER CASES]-----											
70	010000	010000	000001	100000	000010	010000	010000	4(100)	4(100)	PASS	corner_1_two_equal_median
80	001000	000100	001000	010000	000001	001000	001000	3(011)	3(011)	PASS	corner_2_middle_dominates
90	100000	010000	010000	001000	000001	010000	010000	4(100)	4(100)	PASS	corner_3_top_heavy

SUMMARY: PASS (9/9)											

III. Waveform Analysis

(20= 100000, 10=010000, 08=001000, 04=000100, 02=000010, 01=000001)

a0[5:0] =20	20	a0 = 100000	a1 = 100000	a2 = 010000
a1[5:0] =20	20	a3 = 000100	a4 = 000001	
a2[5:0] =10	10	out = 010000		
a3[5:0] =04	04	main_1_example_from_TA		
a4[5:0] =01	01			
out[5:0] =10	10			

a0[5:0] =01	01		
a1[5:0] =02	02		
a2[5:0] =04	04		
a3[5:0] =08	08		
a4[5:0] =10	10		
out[5:0] =04	04		

a0 = 000001 a1 = 000010 a2 = 000100
a3 = 001000 a4 = 010000
out = 000100
main_2_sorted_unique

a0[5:0] =04	04		
a1[5:0] =04	04		
a2[5:0] =04	04		
a3[5:0] =20	20		
a4[5:0] =01	01		
out[5:0] =04	04		

a0 = 000100 a1 = 000100 a2 = 000100
a3 = 100000 a4 = 000001
out = 000100
main_3_clear_middle_repeat

a0[5:0] =01	01		
a1[5:0] =01	01		
a2[5:0] =01	01		
a3[5:0] =01	01		
a4[5:0] =01	01		
out[5:0] =01	01		

a0 = 000001 a1 = 000001 a2 = 000001
a3 = 000001 a4 = 000001
out = 000001
edge_1_all_same_lowest

a0[5:0] =20	20		
a1[5:0] =20	20		
a2[5:0] =20	20		
a3[5:0] =20	20		
a4[5:0] =20	20		
out[5:0] =20	20		

a0 = 100000 a1 = 100000 a2 = 100000

a3 = 100000 a4 = 100000

out = 100000

edge_2_all_same_highest

a0[5:0] =01	01		
a1[5:0] =02	02		
a2[5:0] =04	04		
a3[5:0] =08	08		
a4[5:0] =20	20		
out[5:0] =04	04		

a0 = 000001 a1 = 000010 a2 = 000100

a3 = 001000 a4 = 100000

out = 000100

edge_3_wide_spread

a0[5:0] =01	10		
a1[5:0] =02	10		
a2[5:0] =04	01		
a3[5:0] =08	20		
a4[5:0] =20	02		
out[5:0] =04	10		

a0 = 010000 a1 = 010000 a2 = 000001

a3 = 100000 a4 = 000010

out = 010000

corner_1_two_equal_median

a0[5:0] =01	08	
a1[5:0] =02	04	
a2[5:0] =04	08	
a3[5:0] =08	10	
a4[5:0] =20	01	
out[5:0] =04	08	

a0 = 001000 a1 = 000100 a2 = 001000

a3 = 010000 a4 = 000001

out = 001000

corner_2_middle_dominates

a0[5:0] =01	20	
a1[5:0] =02	10	
a2[5:0] =04	10	
a3[5:0] =08	08	
a4[5:0] =20	01	
out[5:0] =04	10	

a0 = 100000 a1 = 010000 a2 = 010000

a3 = 001000 a4 = 000001

out = 010000

corner_3_top_heavy

IV.Circuit Analysis

For circuit analysis, since both designs were written in behavior level, we used open source program Yosys to synthesize the circuit and estimate the amount of logic gates used.

Terminal Output:

```

=== median ===

+-----Local Count, excluding submodules.
|
136 wires
166 wire bits
 6 public wires
36 public wire bits
 6 ports
36 port bits
136 cells
 49 $_ANDNOT_
  9 $_AND_
  6 $_NAND_
  3 $_NOR_
  1 $_NOT_
  7 $_ORNOT_
  6 $_OR_
 13 $_XNOR_
 42 $_XOR_

```

III. Experience and Reflection

Designing the voting and median circuits helped me understand how to turn problem rules into clear combinational logic. In voting, I learned to count one-hot bits across inputs, compare candidate counts, and enforce tie-breaking priority in a deterministic way. In median, I used histogram and prefix-sum logic to find the first value where cumulative count reaches the middle position, which is a clean hardware-friendly way to compute the median of five inputs. I also used Cursor AI to generate an alternative version of each module to compare as a secondary design.

Building thorough testbenches, including directed and all-case testing, was just as important as the RTL itself because it exposed corner cases and confirmed correctness. Overall, this work improved my ability to structure logic step by step, verify behavior systematically, and think about both function and robustness in digital design.

During the circuit analysis part, I realized I couldn't count the amount of logic gates since I was using behavior level coding, so I had to learn a new open source program Yosys. I am very proud that I have the ability to find open source tools and learn how to use them on my own.